



南京邮电大学
Nanjing University of Posts and Telecommunications

电工电子实验报告

课程名称： 电工电子实验（二）
可编程器件的应用及数字系统设计
实验项目： （状态机）
小型数字系统设计（一）

学 院： 贝尔英才学院
班 级：
学 号：
姓 名：
学 期： 2022-2023学年第1学期

可编程器件的应用及数字系统设计（状态机）

一、实验目的

1. 使用ISE软件完成时序逻辑电路的设计输入并仿真。
2. 掌握Testbench中时序逻辑测试文件的写法。
3. 下载并测试实现的逻辑功能。

二、实验仪器

ISE Design Suite 14.7

三、实验原理

Mealy型有限状态机的状态转移表

现态	次态		输出	
	X=0	X=1	X=0	X=1
S0	S0	S1	0	1
S1	S1	S2	0	1
S2	S2	S3	0	1
S3	S3	S0	1	0

四、实验内容

1. 通过状态机方法重新设计交通灯电路，并讨论有限状态机的不同实现方式和编码方式的特点(参考5.5.5节)，完成设计模块，Testbench，并保存仿真波形，Testbench能够测试到电路设计要求的所有功能，下载到FPGA，完成硬件调测并实现电路功能。

2. 根据交通灯的设计方法，设计一个PWM信号方波发生器，要求如下：

- (1) 输入时钟脉冲频率为100kHz。
- (2) 产生PWM信号的周期为1ms
- (3) PWM信号占空比为10%~90%可变。
- (4) 按键控制占空比步进，1%连续可调。

完成设计模块，Testbench，并保存仿真波形，Testbench能够测试到电路设计要求的所有功能，下载到FPGA，完成硬件调测并实现电路功能。

3. 设计一组交通灯，东西南北两组灯，东西亮红灯18秒，南北亮绿灯15秒，亮黄灯3秒，然后切换东西绿灯15秒，黄灯3秒南北红灯18秒。

五、实验数据

1. 通过状态机方法重新设计交通灯电路，并讨论有限状态机的不同实现方式和编码方式的特点(参考5.5.5节)，完成设计模块，Testbench，并保存仿真波形，Testbench能够测试到电路设计要求的所有功能，下载到FPGA，完成硬件调测并实现电路功能。

- (1) 设计代码

```

module traffic_lights3(clk,rst,cnt_out,count_red,count_green,count_yellow,red,green,yellow
);
input clk,rst;
output reg [5:0] cnt_out;
output reg red,green,yellow;
output reg [4:0] count_red,count_green,count_yellow;
reg [1:0] CS,NS;
parameter IDLE=2'b00,s1=2'b01,s2=2'b10,s3=2'b11;
always@(posedge clk or negedge rst)
begin
    if(!rst)
        cnt_out<=0;
    else if(cnt_out==6'b100100)
        cnt_out<=1;
    else
        cnt_out<=cnt_out+1;
end

always@(posedge clk or negedge rst)
begin
    if(!rst)
        CS<=IDLE;
    else
        CS<=NS;
end

always@(rst or CS or cnt_out)
begin
    case(CS)
        IDLE:begin NS<=s1;end
        s1:begin if(cnt_out==6'b010010)
                NS<=s2;
                else
                NS<=s1;
                end
        s2:begin if(cnt_out==6'b100001)
                NS<=s3;
                else
                NS<=s2;
                end
    endcase
end

```

```

        s3:begin if(cnt_out==6'b100100)
            NS<=s1;
        else
            NS<=s3;
        end
        default: begin NS<=IDLE; end
    endcase
end
always@(posedge clk or negedge rst)
begin
    if(!rst)
        {red,green,yellow}<=3'b000;
    else
        begin
            {red,green,yellow}<=3'b000;
            case(NS)
            IDLE:begin {red,green,yellow}<=3'b000;
                count_red<=5'b10010;
                count_green<=5'b01111;
                count_yellow<=5'b00011;
            end
            s1:begin {red,green,yellow}<=3'b100;
                count_red<=count_red-1;
                count_green<=5'b01111;
                count_yellow<=5'b00011;
            end
            s2:begin {red,green,yellow}<=3'b010;
                count_red<=5'b10010;
                count_green<=count_green-1;
                count_yellow<=5'b00011;
            end
            s3:begin {red,green,yellow}<=3'b001;
                count_red<=5'b10010;
                count_green<=5'b01111;
                count_yellow<=count_yellow-1;
            end
            default:begin {red,green,yellow}<=3'b000;
                end
            endcase
        end
    end
endmodule

```

(2) 测试代码

```

initial begin
    // Initialize Inputs
    clk = 0;
    rst = 0;


    // Wait 100 ns for global reset to finish
    #2 rst=1;

    // Add stimulus here


end
always #5 clk=~clk;
endmodule

```


(3) 仿真结果

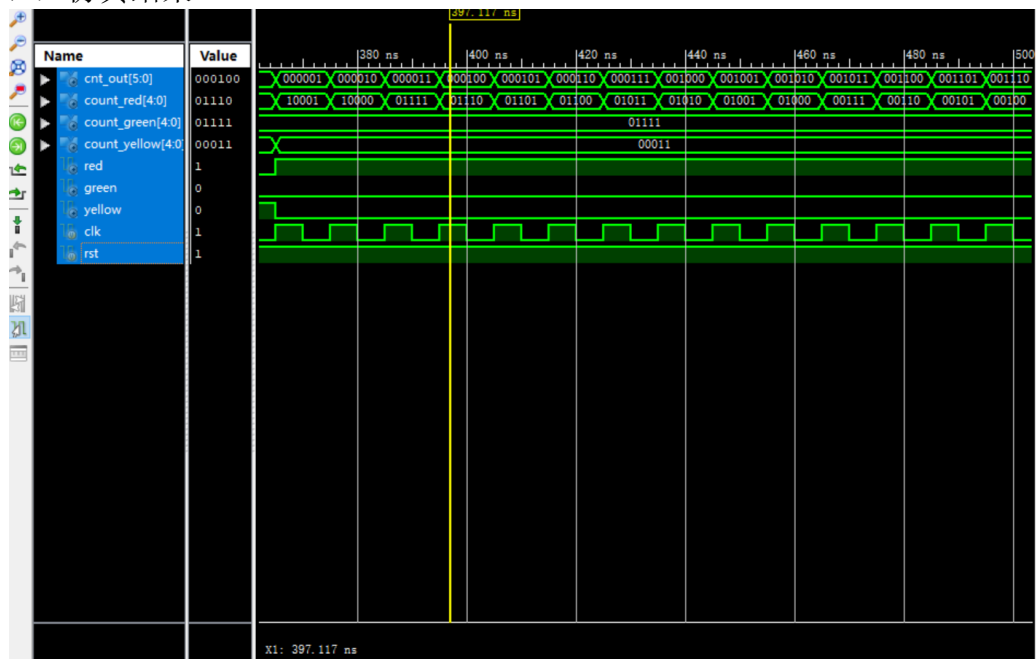


红灯倒计时仿真截图

 

红灯倒计时手绘图

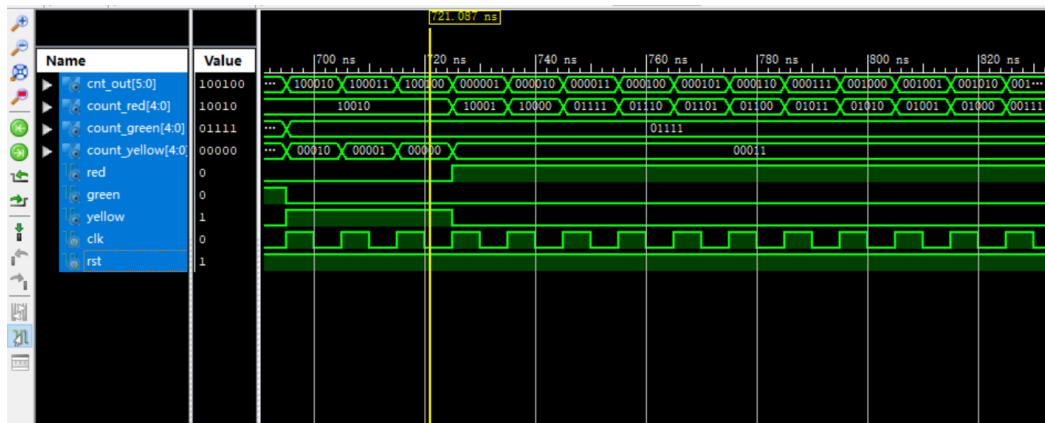


黄灯倒计时仿真截图

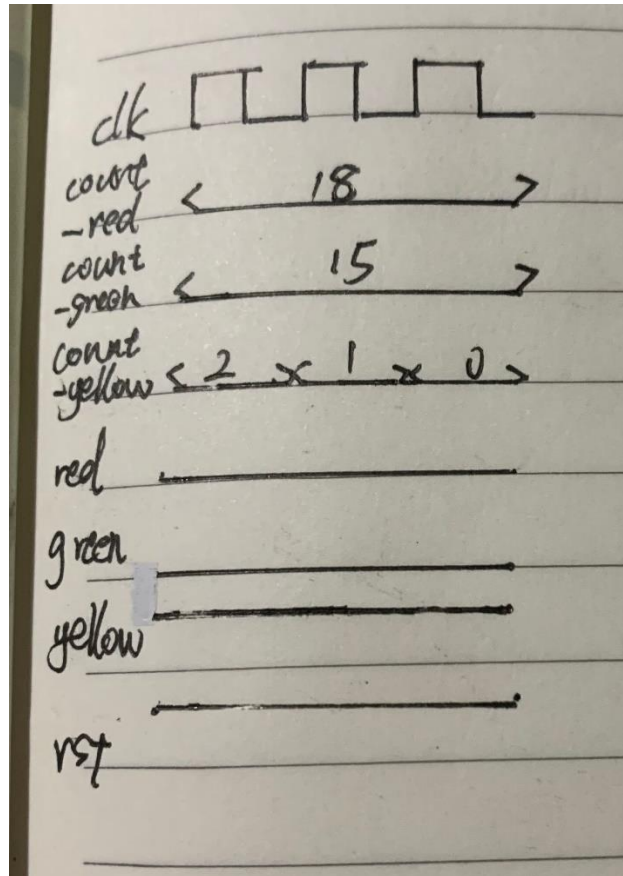

黄灯倒计时手绘图



绿灯倒计时仿真截图

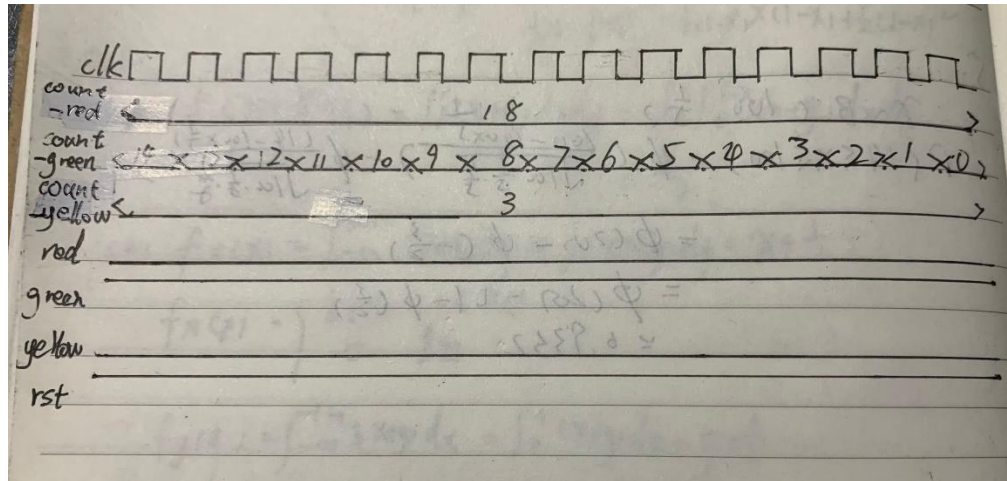

绿灯倒计时手绘图

2. 根据交通灯的设计方法，设计一个PWM信号方波发生器，要求如下：

- (1) 输入时钟脉冲频率为100kHz。
- (2) 产生PWM信号的周期为1ms
- (3) PWM信号占空比为10%~90%可变。
- (4) 按键控制占空比步进，1%连续可调。

完成设计模块，Testbench，并保存仿真波形，Testbench能够测试到电路设计要求的所有功能，下载到FPGA，完成硬件调测并实现电路功能。

(1) 设计代码

```
module pwml(rst,clk,key,pwm
);
input rst,clk,key;
output pwm;
reg [6:0] count;
reg [6:0] pwm_count;
always@(posedge clk or negedge rst)
begin
if(!rst)
count<=0;
else if(rst==7'b1100011)
count<=0;
else
count<=count+1'b1;
end

always@(posedge key or negedge rst)
begin
if(!rst)
pwm_count<=10;
else if(pwm_count==7'b1011010)
pwm_count<=10;
else
pwm_count<=pwm_count+7'b0000001;
end

assign pwm=(count<pwm_count)?1:0;
endmodule
```

(2) 测试代码

```

initial begin
    // Initialize Inputs
    rst = 0;
    clk = 0;
    key = 0;


    // Wait 100 ns for global reset to finish
    #2 rst=1;

    // Add stimulus here


end
always #5 clk=~clk;
always #5 key=~key;
endmodule

```

(3) 仿真结果（截图及手绘）

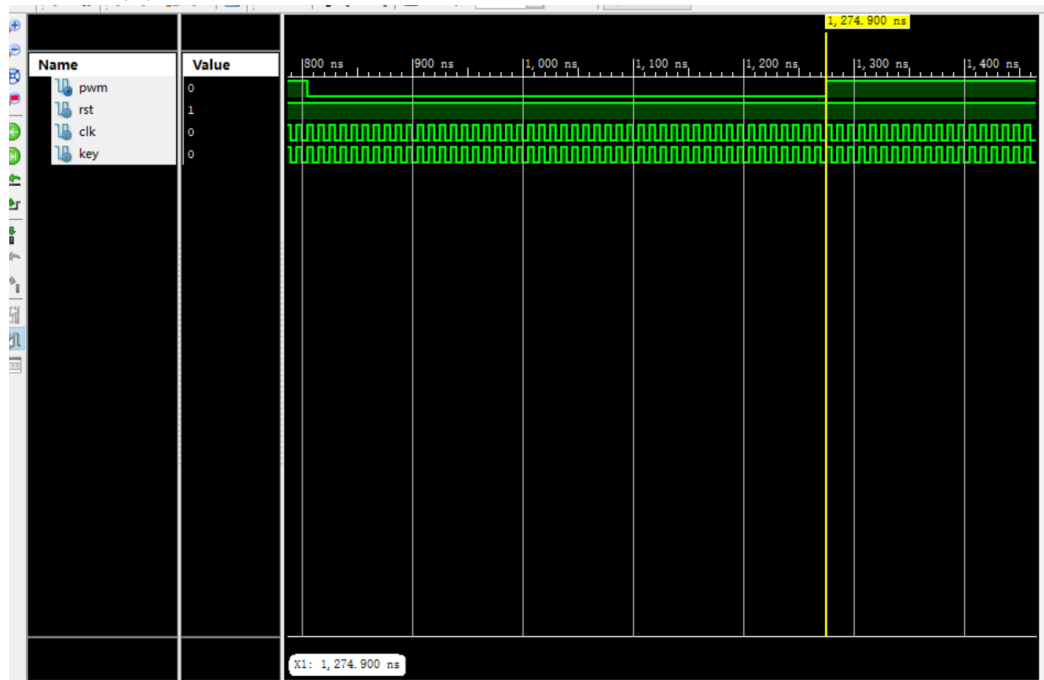

Pwm仿真截图

 

Pwm手绘波形图

3. 设计一组交通灯，东西南北两组灯，东西亮红灯18秒，南北亮绿灯15秒，亮黄灯3秒，然后切换东西绿灯15秒，黄灯3秒南北红灯18秒。

(1) 设计代码

```
module sixlight(clk,rst,cnt_out,count_WEred,count_SNred,count_WEgreen,count_SNgreen,
count_WEyellow,count_SNyellow,WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow
);
input clk,rst;
output reg [5:0] cnt_out;
output reg WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow;
output reg [4:0] count_WEred,count_SNred,count_WEgreen,count_SNgreen,
count_WEyellow,count_SNyellow;
reg [2:0] current_state,next_state;
parameter IDLE=3'b000,s1=3'b001,s2=3'b010,s3=3'b011,s4=3'b100;
always@(posedge clk or negedge rst)
begin
    if(!rst)
        cnt_out<=0;
    else if(cnt_out==6'b100100)
        cnt_out<=1;
    else
        cnt_out<=cnt_out+1;
end

always@(posedge clk or negedge rst)
begin
    if(!rst)
    begin
        current_state<=IDLE;
    end
    else
        current_state<=next_state;
end

always@(rst or current_state or cnt_out)
begin
    case(current_state)
        IDLE:begin next_state<=s1;end
        s1:begin if(cnt_out==6'b001111)
            next_state<=s2;
            else
                next_state<=s1;
            end
        s2:begin if(cnt_out==6'b010010)
```

```

        next_state<=s3;
    else
        next_state<=s2;
    end
s3:begin if(cnt_out==6'b100001)
    next_state<=s4;
else
    next_state<=s3;
end
s4:begin if(cnt_out==6'b100100)
    next_state<=s1;
else
    next_state<=s4;
end
    default: begin next_state<=IDLE; end
endcase
end
always@(posedge clk or negedge rst)
begin
    if(!rst)
        {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b000000;
    else
        begin
            {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b000000;
            case(next_state)
                IDLE:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b000000;
                    count_WEred<=5'b10010;
                    count_SNred<=5'b10010;
                    count_WEgreen<=5'b01111;
                    count_SNgreen<=5'b01111;
                    count_WEyellow<=5'b00011;
                    count_SNyellow<=5'b00011;

                    end
                s1:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b100100;
                    count_WEred<=count_WEred-1;
                    count_SNred<=5'b10010;
                    count_WEgreen<=5'b01111;
                    count_SNgreen<=count_SNgreen-1;
                    count_WEyellow<=5'b00011;
                    count_SNyellow<=5'b00011;

                    end
                s2:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b100001;
                    count_WEred<=count_WEred-1;
                    count_SNred<=5'b10010;
                    count_WEgreen<=5'b01111;
                    count_SNgreen<=5'b01111;
                    count_WEyellow<=5'b00011;
                    count_SNyellow<=count_SNyellow-1;

                    end
                s3:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b011000;
                    count_WEred<=5'b10010;
                    count_SNred<=count_SNred-1;
                    count_WEgreen<=count_WEgreen-1;
                    count_SNgreen<=5'b01111;
                    count_WEyellow<=5'b00011;
                    count_SNyellow<=5'b00011;

                    end
                s4:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b010010;
                    count_WEred<=5'b10010;
                    count_SNred<=count_SNred-1;
                    count_WEgreen<=5'b01111;
                    count_SNgreen<=5'b01111;
                    count_WEyellow<=count_WEyellow-1;
                    count_SNyellow<=5'b00011;

                    end
                default:begin {WEred,SNred,WEgreen,SNgreen,WEyellow,SNyellow}<=6'b000000;
                    end
            endcase
        end
    end
endmodule

```

(2) 测试代码

```

initial begin
    // Initialize Inputs
    clk = 0;
    rst = 0;


    // Wait 100 ns for global reset to finish
    #2 rst=1;

    // Add stimulus here


end

always #5 clk=~clk;
endmodule
    
```

(3) 仿真结果（截图及手绘）

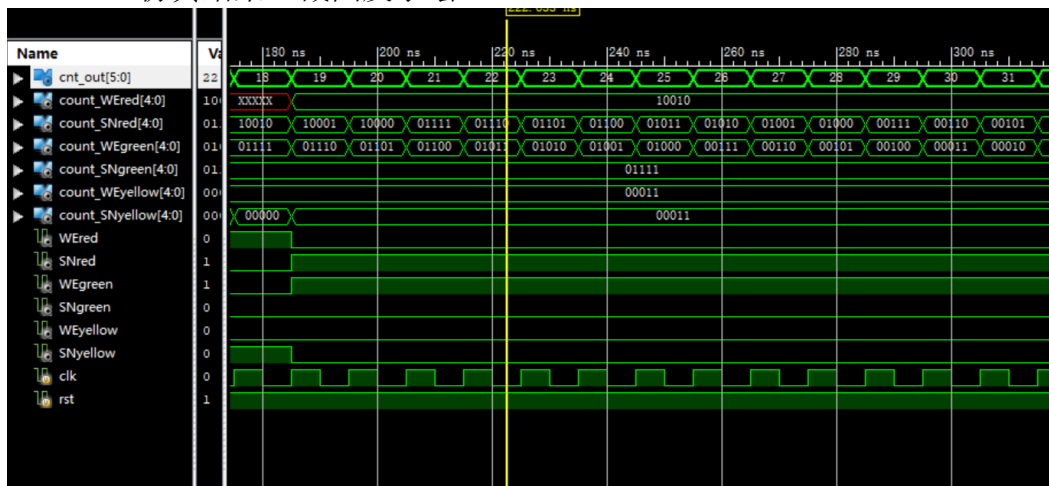


东西方向绿灯黄灯及南北方向红灯倒计时仿真截图

 

东西方向绿灯黄灯及南北方向红灯倒计时手绘波形图



东西方向红灯及南北方向绿灯黄灯倒计时仿真截图

 

东西方向红灯及南北方向绿灯黄灯倒计时手绘波形图

六、实验小结

对三段式有限状态机的设计有了具体的了解，掌握三段式有限状态机中各个always模块分别起的作用，了解了如何运用多个always模块分块对任务进行设计，对Verilog语言的运用有了更深的理解。掌握了Testbench中时序逻辑测试文件的写法。